

Antenna relay 1:4


Frequency range 0-52MHz

Return Loss > 30dB

Antenna relay 1:4

- This relay box was originally built for club station OH1AJ, when its antenna system was renovated in 2018. As multiple copies have been built by other amateurs after that, I publish it also here.
- There is no printed circuit board. The relays are fixed to the box cover plate with double sided tape. Wiring is made with dia 1mm copper wire. The layout is important as stray inductance is the challenge. Additional inductance is compensated with abt 10pF capacitors in the half way between input and output connectors. The capacitors are made out of double sided PCB.
- Good matching is achieved. But it requires trimming of those capacitors. Accurate 50ohm termination is connected to the input terminal (TX). SWR / return loss is measured with network analyzer at each output (Ant). SWR of each output (Ant) is trimmed to minimum by cutting pieces away from the PCB capacitor. See pictures.
- Power capability is the full legal 1.5kW


Antenna relay 1:4, 0-52MHz, RL >30dB

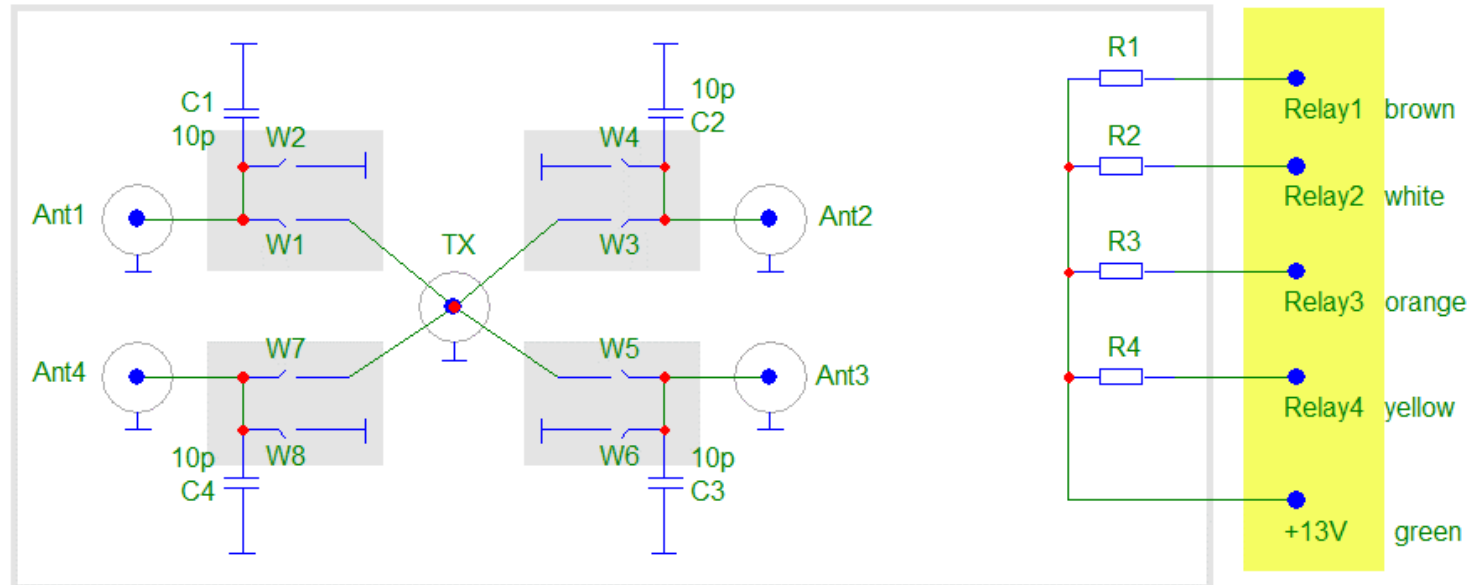


W1-W2 = SPDT
W2, W4, W6, W8 on when relays off

Housing Hammong 1590U, 120x120x55mm, aluminium
Relays SPDT 16A 250V 12VDC like Schrack RT314-12
Capacitors C1-C4 = double sided printed circuit board, 1.5mm glas fiber, size 17x20mm


26.9.2018
OH1TV

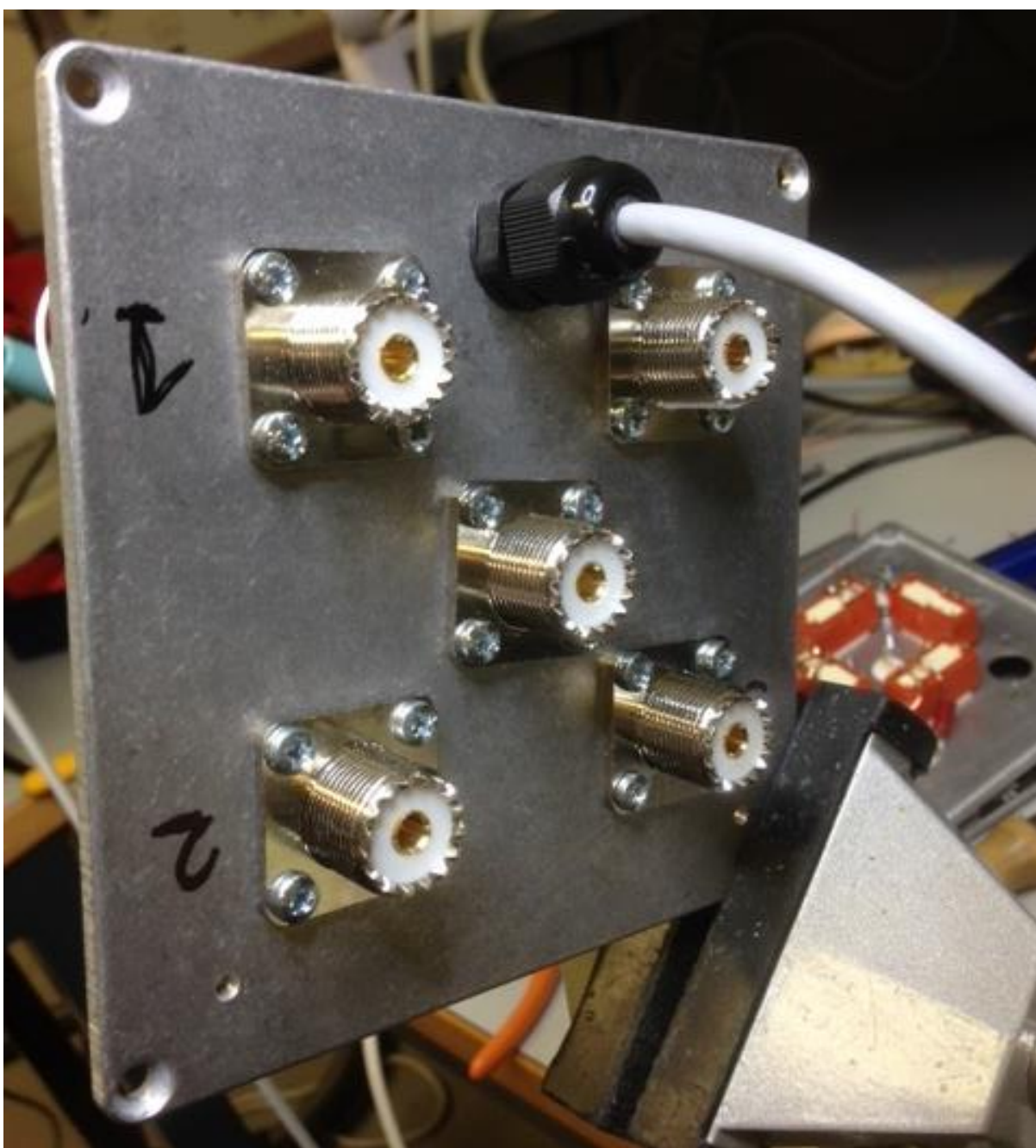


Pigtail cable 2m long

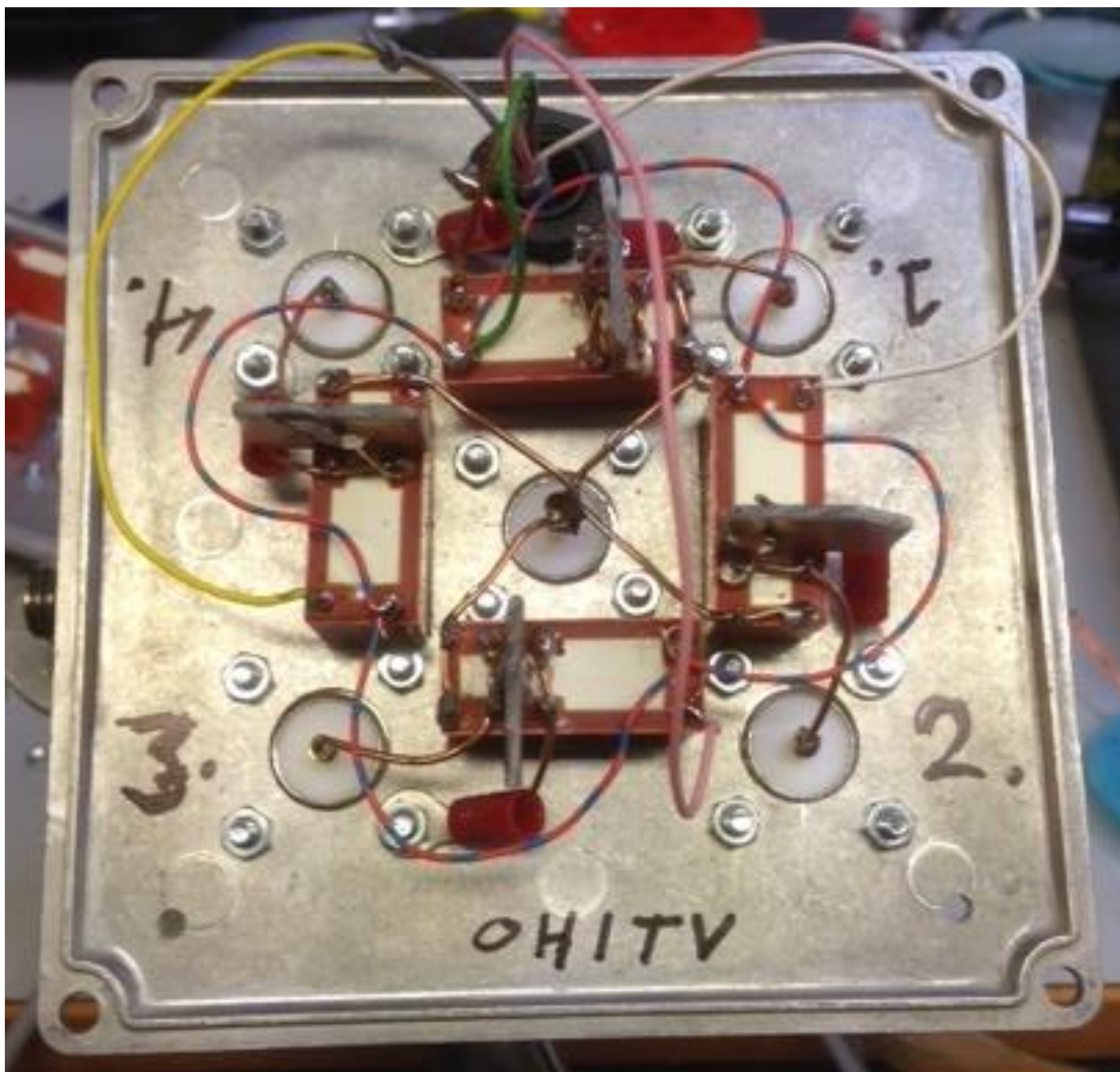

Wire dia 1mm CU non
emaled clear

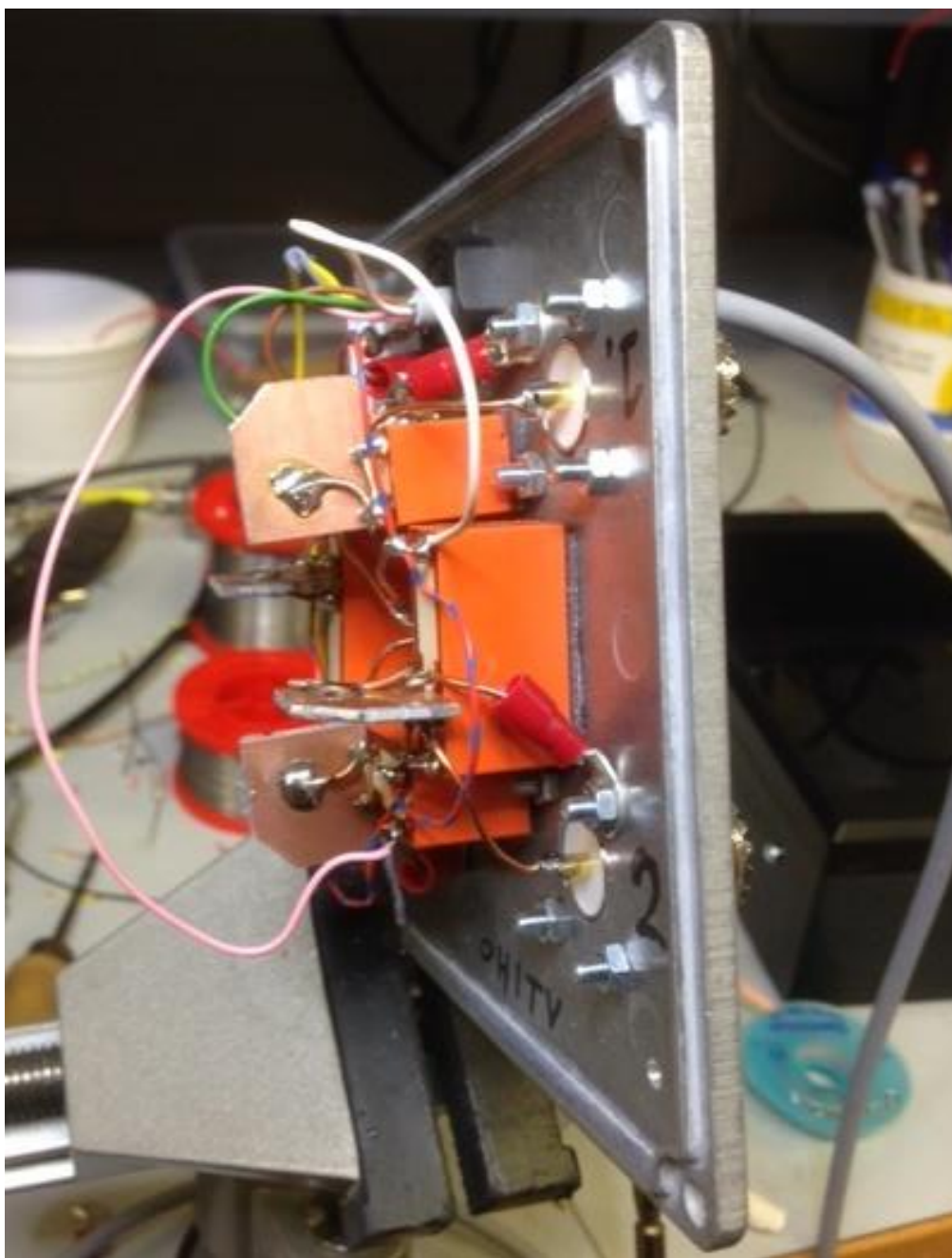


Antenna relay box 1:4

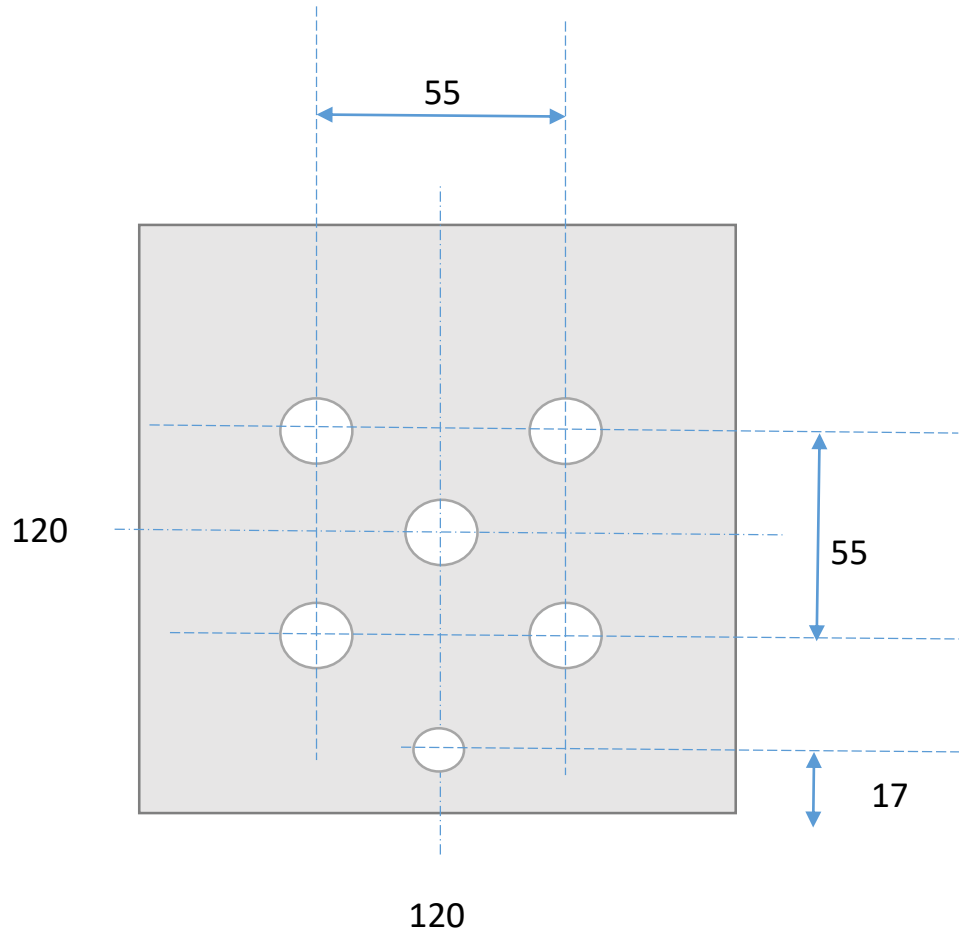

- The box is Hammond 1590U
- All components are mounted on the cover plate
- 5pcs UHF female connectors, flange mount

Min SWR = 1.00 @ 3.400 MHz

AVG= 4

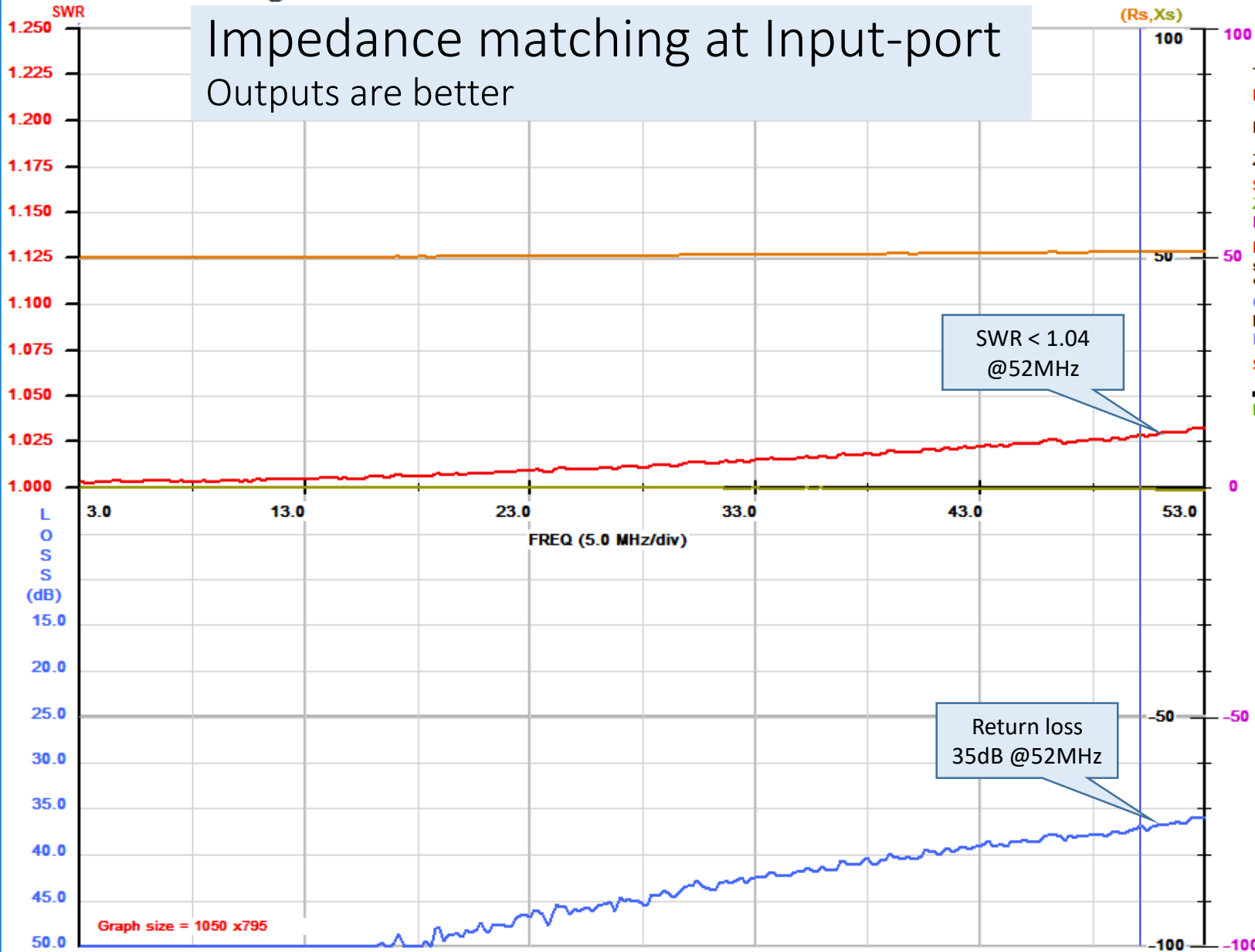

Impedance matching at Input-port
Outputs are better

SWR < 1.04
@ 52MHz

Return loss
35dB @ 52MHz

Freq = 50.114
 Freq Step = 0.200
 Zref = 50.000
 SWR = 1.029
 Zmag = 51.388
 Phase = -0.424
 Rho Mag=0.0142
 s11= 0.0137 - j0.0037
 % refl power = 0.0
 Output = 100%
 DC Voltage = 1000.00
 Return Loss= 36.97dB

Short/Open Circuit:
 Cable Loss= 18.48dB

Equivalent Circuit:
 Rs = 51.386
 Xs = -0.380
 Q = 0.0
 Cs = 0.00835 uF

Rp = 51.389
 Xp = -6945.660
 Cp = 0.457 pF

Gp = 0.019459
 Bp = -0.000144